

Errata

zadnja dopolnitev: 24. april 2001
(<http://paris.fe.uni-lj.si/lsd/skripte/skripte.htm>)

Str. 20, Naloga 3.5

$$R_2 = \frac{U_{EE} - U_{D1} - U_{D2}}{I_{E20}} = 2933 \Omega.$$

Str. 22

1) Izberemo I_{C0} in s tem določimo strmino $g_{21E} = \frac{q}{kT} I_{C0} = \frac{I_{C0}}{U_T}$.

Str. 24

8) Določimo C_{V2} iz pogoja $\omega_{C_{V2}} \leq \frac{1}{10} \omega_{C_E}$: $C_{V2} \geq \frac{1}{\frac{1}{10} \omega_m (R_C \parallel \frac{1}{g_{22E}} + R_L)}$.

Str. 24

1) Izberemo I_{C0} in s tem določimo strmino $g_{21E} = \frac{q}{kT} I_{C0} = \frac{I_{C0}}{U_T}$.

Str. 26

1) Izberemo I_{C0} in s tem določimo strmino $g_{21E} = \frac{q}{kT} I_{C0} = \frac{I_{C0}}{U_T}$.

Str. 27

7) Določimo C_{V1} iz pogoja $\omega_{C_{V1}} \leq \frac{1}{10} \omega_m$:

8) Določimo C_{V2} iz pogoja $\omega_{C_{V2}} \leq \frac{1}{10} \omega_m$:

$$C_{V2} \geq \frac{1}{\frac{1}{10} \omega_m (R_C \parallel (1/g_{22E} + R_E) + R_L)} \quad \text{za } C_{V1} \text{ kot odprte sponke pri } \omega = \omega_{C_{V2}}$$

Str. 28, Naloga 4.1

Med podatki manjka: $U_{BE0} = 0.7 \text{ V}$ in $\frac{kT}{q} = 25 \text{ mV}$

Str. 29, Naloga 4.2

Med podatki manjka: $R_G = 50 \Omega$

Str. 30, Naloga 4.2

$$g_{21E} = \frac{q}{kT} I_{C0} = 20 \text{ mS}$$

$$C_E = \frac{1}{2\pi f_m (R_3 + R_E \parallel \frac{r_{11E} + R_1 \parallel R_2 \parallel R_G}{1 + \beta_{AC}})} = 7.55 \mu\text{F}$$

$$C_{V1} \geq \frac{1}{\frac{1}{10} \omega_m (R_G + R_1 \parallel R_2 \parallel r_{vhAC})} = \frac{1}{\frac{2\pi f_m}{10} (R_G + R_1 \parallel R_2 \parallel (r_{11E} + (1 + \beta_{AC}) R_E))} = 844 \text{ nF.}$$

Str. 41, Naloga 5.3

$$R_G + r_{BB'} + R_e \leq \frac{k_E r_{B'E} \cdot 382.5 \Omega}{k_E r_{B'E} - 382.5 \Omega} = 423 \Omega \quad \text{in zato} \quad \underline{\underline{R_G \leq 369 \Omega}}$$

Str. 42, Naloga 6.1

Med podatki napaka: $\omega_0 = 10^8 \text{ rad/s}$

Str. 44, Naloga 6.2

$$A_U(\omega = \omega_0) = A_0 = -\frac{|y_{21}|}{g_{22} + g_{pL}} = -1500$$

Str. 48, Naloga 6.5

$$L_1 = L_2 = \frac{1}{\omega_0 g_{pL} Q_L} = \frac{\frac{1}{Q_{ef}} - \frac{1}{Q_{0k}}}{\omega_0 (g_{22} + g_{11}^*)} = 9.7 \mu\text{H}$$

Str. 49, Naloga 6.5

$$C_2 = \frac{1}{\omega_0^2 \cdot L_1 \cdot n_1} = 130.5 \text{ pF} \quad \text{in} \quad C_1 = \frac{n_1}{1 - n_1} C_2 = 32.6 \text{ pF}$$

$$C_4 = \frac{1}{\omega_0^2 \cdot L_2 \cdot n_2} = 130.5 \text{ pF} \quad \text{in} \quad C_3 = \frac{n_2}{1 - n_2} C_4 = 32.6 \text{ pF}$$

Str. 49, Naloga 6.6

Med podatki napaka: $y_{21} = g_{21} = 20 \text{ mS}$

Med podatki napaka: $L_2 = 0.3 \mu\text{H}$

Med podatki manjka: $R_L = 2 \text{ k}\Omega$

Str. 50, Naloga 6.5

$$C_{BC \text{ kritični}} = \frac{2G_1 G_2}{\omega_0 |y_{21}|} = \frac{2(g_{k1} + g_{11})(g_{k2} + g_{22} + G_L^*)}{\omega_0 g_{21}} = 2.04 \text{ pF}$$

Str. 50, Naloga 6.7

$g_{11E} = 0.5 \text{ mS}$

Str. 51, Naloga 6.7

$G_L = g_{22}(1 + m_2) = 38.4 \mu\text{S}$

$$A_{MUG} = \frac{P_L}{P_{vh \text{ max}}} = \frac{g_{21}^2}{4g_{11}g_{22}} \cdot \frac{16m_2}{(1 + m_1)^2(1 + m_2)^2} = \frac{g_{21}^2}{g_{11}g_{22}} \cdot \frac{4m}{(1 + m)^4} = 4179.7$$

Str. 52, Naloga 6.8

$$P_L = \frac{1}{2} \frac{g_{21}^2 U_1^2 n^2}{(g_{22} + g_k + n^2 G_L)^2} \cdot G_L = \frac{1}{2} \frac{I_1^2}{(g_{11} + G_G)^2} \cdot \frac{g_{21}^2}{(g_{22} + g_k + n^2 G_L)^2} \cdot n^2 G_L$$

$$m_2 = \frac{G_L^*}{g_{22} + g_k} = \frac{n^2 G_L}{g_{22} + g_k} = 0.6$$

$$A_{MUG} = \frac{P_L}{P_{vh \text{ max}}} = \frac{g_{21}^2}{g_{11}(g_{22} + g_k)} \cdot \frac{4m_2}{(1 + m_1)^2(1 + m_2)^2} = 3125$$

Str. 54, Naloga 7.1

$$R_{v_{hT_1 DC}} = r_{11E} + (\beta + 1)R_E = 103.5 \text{ k}\Omega$$

Str. 58, Naloga 8.1

$$U_{CE0} = +U_{BE0} + U_{CC} - R_{C0}I_{C0} = +U_{BE0} + U_{CC} - R_{C0}I_{RE0} / 2 = \underline{\underline{+7.6 \text{ V}}}.$$

Str. 59, Naloga 8.1

$$R_{v_{hs}} = r_{11E} + (\beta_{AC} + 1)2R_E = \underline{\underline{4.59 \text{ M}\Omega}}$$

Str. 60, Naloga 8.2

$$A_{sp} = -0.0445$$

Str. 61, Naloga 8.2

$$CMRR = \left| \frac{A_d}{A_{sp}} \right| = 5353 \quad \text{ozroma} \quad \underline{\underline{CMRR = 74.6 \text{ dB}}}.$$

Str. 62, Naloga 8.4

Med podatki manjka : $\beta = 100$

Str. 67, Naloga 8.9

$$CMRR = \frac{A_d}{A_{sp}} = 10^{\frac{68 \text{ dB}}{20 \text{ dB}}} = 2511.9$$

Str. 72, Naloga 8.13

$$A_{U1} = -g_{21E} (R_{C1} \parallel (R_{vh2} / 2)) \cong -69.5.$$

$$A_U = A_{U1} A_{U2} A_{U3} \cong \underline{\underline{4358}}.$$

Str. 76, Naloga 9.2

Prvi O.O. v narisnem vezju mora imeti (-) in (+) vhodni sponki zamenjani.

Str. 79, Naloga 9.4

$$I_B^- = \frac{u_{izh}}{R} - \left(\frac{R}{R_s^-} + 1 \right) \cdot \frac{U_{off}}{R} = \frac{u_{izh}}{R} \left[1 - \left(\frac{1}{R_s^-} + \frac{1}{R} \right) \cdot \frac{RU_{off}}{u_{izh}} \right] = \frac{u_{izh}}{R} [1 - \delta]$$

Str. 80, Naloga 9.5

$$u^+ = u_s + \frac{u_d}{2} = u_s \left(1 - \frac{1}{2 \cdot CMRR} \right) - \frac{U_{off}}{2} + \frac{u'_d}{2} = u_s - \frac{U_{off}}{2} = -R_3 i^+$$

Str. 81, Naloga 9.5

$$u_{izh} \cong \frac{R_1 + R_2}{R_1} U_{off} + R_2 I_{off} = \pm 303 \text{ mV} \pm 20 \text{ mV}$$

Str. 81, Naloga 9.5

Med podatki napaka: $I_{off} = -100 \text{ nA}$

Str. 93, Naloga 10.2

$$R_{izh\beta} \leq \frac{R_{izh}}{1 + A_{U0 \min}} = 0.0015 \Omega$$

Str. 99, Naloga 10.6

ki se z naraščajočo A_0 giblje od vrednosti -0.0095 proti -0.01 , kamor limitira, ko gre ojačenje $A_0 \rightarrow \infty$.

Str. 127, Naloga 12.7

$$u_{izh2}(t) = U^+ + u_c(t) = U^+ - \frac{1}{R_1 C} \int (u_{izh1}(t) - U^+) dt .$$

$$U_{ZTP} - U_{STP} = U^+ - \frac{1}{R_1 C} \int_{t_0}^{t_0+t_r} (-U_{sat} - U^+) dt = U^+ - \frac{1}{R_1 C} (-U_{sat} - U^+) t_r ,$$

$$t_r = -R_1 C \frac{U_{ZTP} - U_{STP} - U^+}{-U_{sat} - U^+} = 457.4 \mu s .$$

$$t_f = -R_1 C \frac{U_{STP} - U_{ZTP} - U^+}{+U_{sat} - U^+} = 116.4 \mu s .$$

$$T = t_r + t_f = 573.8 \mu s .$$