


ANALOG ELECTRONIC CIRCUITS

Laboratory work


Exercise 7 – Differential amplifier

 Task:


- Design and construct differential amplifier with transfer function $u_{izh} - U_{REF} = A_d \cdot u_d$.



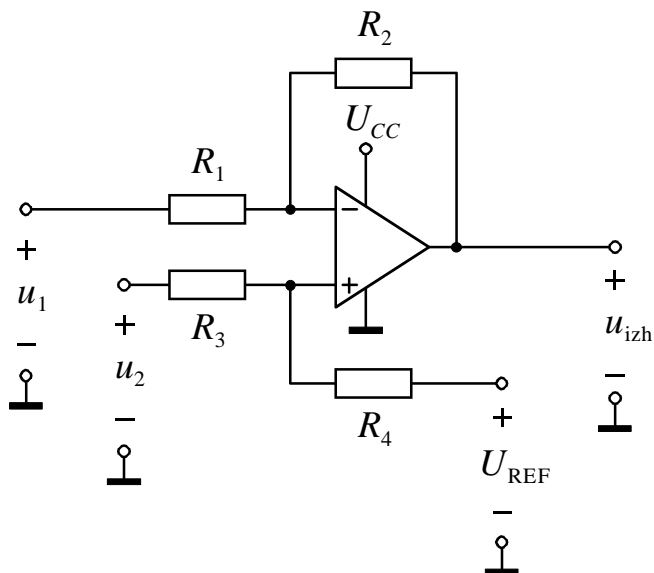- Use a single power supply $U_{CC} = 20$ V and operational amplifier of type 741 and the proposed topology. Differential voltage amplification should be set to $A_d = 20$; ($u_d = u_2 - u_1$).



 - Use the proposed circuit to generate reference voltage $U_{REF} = 5$ V.



Calculation of component value:

Component values:

$R_1 =$

$R_5 =$

$R_2 =$

$R_6 =$

$R_3 =$


$C_6 =$

$R_4 =$

Amplification measurements:

- Measure differential-mode amplification
 $A_d = u_{izh} / u_d$ (u_d : sine signal, $U_0 = 100 \text{ mV}$, $f = 10\text{kHz}$).
- Measure common-mode amplification $A_s = u_{izh} / u_s$ (u_s : sine signal, $U_0 = 1 \text{ V}$, $f = 10\text{kHz}$).
- While measuring A_d and A_s observe the alternating component of the input and output signal. Reference potential for the measurement of u_{izh} is U_{REF} and not GND!
- Obtain CMRR


Differential-mode amplification:

 

$$A_d = u_{izh} / u_d =$$

$$A_d = \qquad \qquad \qquad A_d = \qquad \qquad \qquad \text{dB}$$

Common-mode amplification:

 

$$A_s = u_{izh} / u_s =$$

$$A_s = \qquad \qquad \qquad A_s = \qquad \qquad \qquad \text{dB}$$


CMRR:

$$\text{CMRR} = A_d / A_s =$$

$$\text{CMRR} = \qquad \qquad \qquad \text{CMRR} = \qquad \qquad \qquad \text{dB}$$


Gain measurements of a real signal:

Real excitation of the amplifier will be simulated by using a DC power source U_{SIG} , which represents a useful signal, and function generator u_{dist} , which represents common-mode disturbance (see figure below).

 

Measurement 1:

 Set the voltage of useful signal to $U_{\text{SIG}} = 20 \text{ mV}$. Disturbance signal u_{dist} should be represented as a sine signal with frequency of 10 kHz. Change the amplitude of the disturbance signal from 0 V to 3 V in steps of 1 V. Draw all four waveforms of the output signal to the graph.




- Increase the amplitude of the disturbance u_{dist} and find out at which value the amplifier stops working properly. What happens in the circuit at that value?

$U_{\text{dist max}} =$

Measurement 2:

 Set the amplitude of sine disturbance to 2 V and frequency to 10 kHz. Change the voltage of useful signal U_{SIG} from 0 V to 60 mV in steps of 20 mV. Draw all four waveforms of the output signal to the graph.



- Increase the amplitude of the useful signal U_{SIG} and find out at which value the amplifier stops working properly. What happens in the circuit at that value?

$U_{\text{SIG max}} =$