
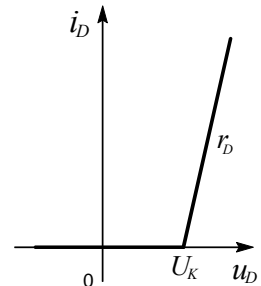


Written exam at the course
NONLINEAR ELECTRONIC CIRCUITS
 II. degree – 1. class / APS, 14. 2. 2023

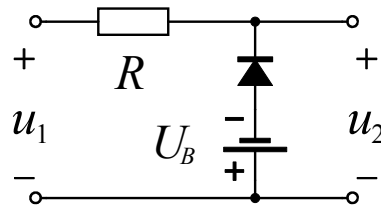1. Calculate and draw the transfer function $u_2(u_1)$ for the drawn circuit! What is the peak-to-peak value of output voltage U_{2pp} , if input equals $u_1(t) = 5 \text{ V} \cdot \sin(\omega t)$?


$U_B = 2,5 \text{ V}$
 $R = 100 \ \Omega$
 $r_D = 10 \ \Omega$
 $U_K = 0,7 \text{ V}$



(Solution: $u_2 = u_1$; $u_1 \geq -3,2 \text{ V}$, $u_2 = 1/11 \cdot u_1 + 32/11 \text{ V}$; $u_1 < -3,2 \text{ V}$; $U_{2pp} = 8,36 \text{ V}$)


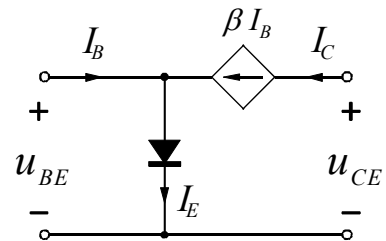
2. Draw a circuit of a simple voltage stabilizer consisting of an *npn* transistor, a breakdown diode and a resistor with the parameters given. Consider the specified transistor model for the active region. Replace the diode in the model with a battery $U_{BE} = 0,6 \text{ V}$ and a series resistance $R_E = 0,1 \ \Omega$. The stabilizer operates in the input voltage range $12 - 24 \text{ V}$. Determine the output voltage at the input voltage of 24 V , maximum power on the transistor and output resistance at output current of $0,5 \text{ A}$.

$U_{z0} = 5,6 \text{ V}$
 $r_z = 10 \ \Omega$
 $R = 470 \ \Omega$
 $\beta = 50$




(S.: $U_{izh-out} = 5,23 \text{ V}$, $R_{izh-out} = 0,292 \ \Omega$, $P_T \approx 9,39 \text{ W}$, $P_T = 9,21 \text{ W}$)

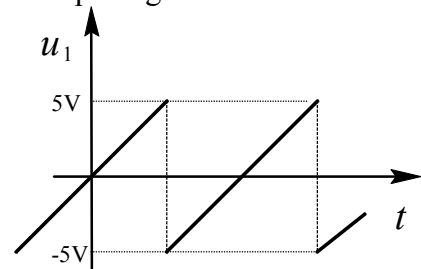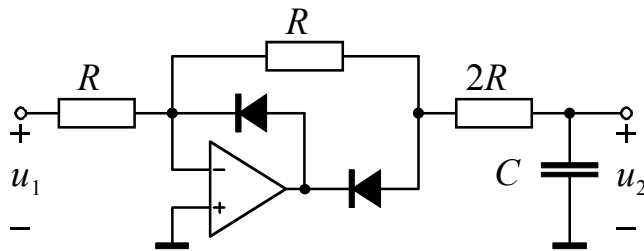3. Calculate the output voltage u_2 at the given input signal u_1 . Simplify the calculation by assuming that the polarization of the diodes depends only on the input signal. Complement the circuit to get the true mean voltage detector of half-wave rectified input signal. $C \rightarrow \infty$



(Solution: $U_2 = -1,5 \text{ V}$, diode anti-parallel to the right diode)

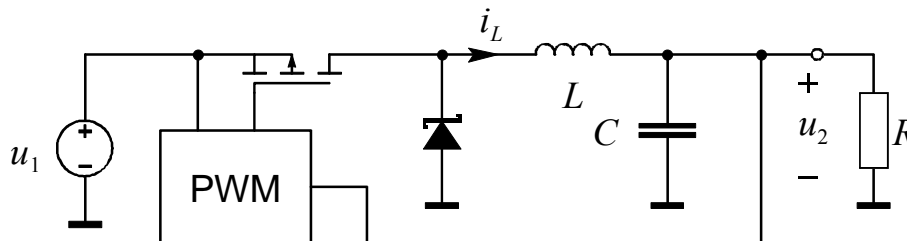4. The switch regulator in the schematics below is designed for output voltage $U_2 = 5 \text{ V}$. The input voltage U_1 changes in the range of $10 - 15 \text{ V}$. Determine the inductance, so that the regulator already operates in continuous current mode at load current of 1 A . Assume the transistor to be ideal, for the diode use knee voltage of $U_K = 0,3 \text{ V}$. What will be the maximum losses on the diode at the load current 2 A ? $f = 130 \text{ kHz}$



(Solution: $U_1 = 15 \text{ V}$; $D = 0,346$, $\Delta I_L = 2 \text{ A}$, $L_{min} = 9,89 \ \mu\text{H}$, $P_D = 0,392 \text{ W}$)

You have 75 minutes, the use of a sheet with basic equations is allowed.
 The results are expected to be published tomorrow in STUDIS.