
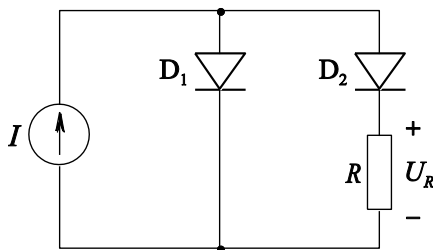


Written exam »Semiconductor Devices«
(30. 8. 2012)

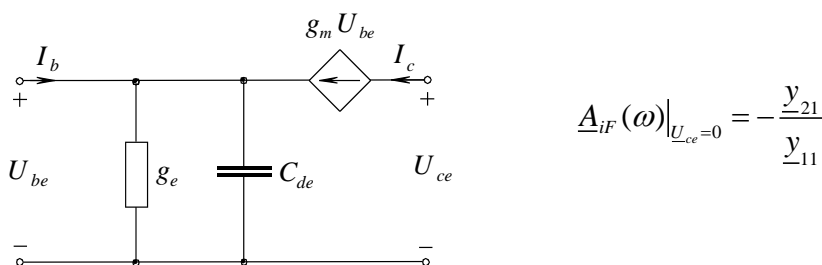
1. Silicon p^+n -junction ($N_A \gg N_D$) has breakdown voltage $U_{BR} = 250$ V, at forward bias voltage $U = 0,6$ V conducts $I = 1$ mA. Calculate concentration of doping in lower-doped layer and area of pn-junction. Other data: $\tau_p = 0,1$ μ s in n -layer, $\mu_p = 400$ $\text{cm}^2/(\text{Vs})$. Breakdown voltage occurs, when the electric field at the junction reaches 400 kV/cm. In calculation you can neglect the diffusion voltage U_D .
2. Calculate R in given circuit, so that $U_R = 50$ mV. Diodes are identical, DC source current is $I = 10$ mA.



3. Calculate short-circuit current amplification $A_{iF}(\omega, U_{ce} = 0)$ of bipolar transistor in orientation CE for small signals with frequency $\omega = 10^6$ rads^{-1} . Data: $\alpha_0 = 0,99$, $g_e = 25$ mS, $C_{de} = 200$ pF. Calculate also ω_T . ($g_m = \alpha_0 g_e$)



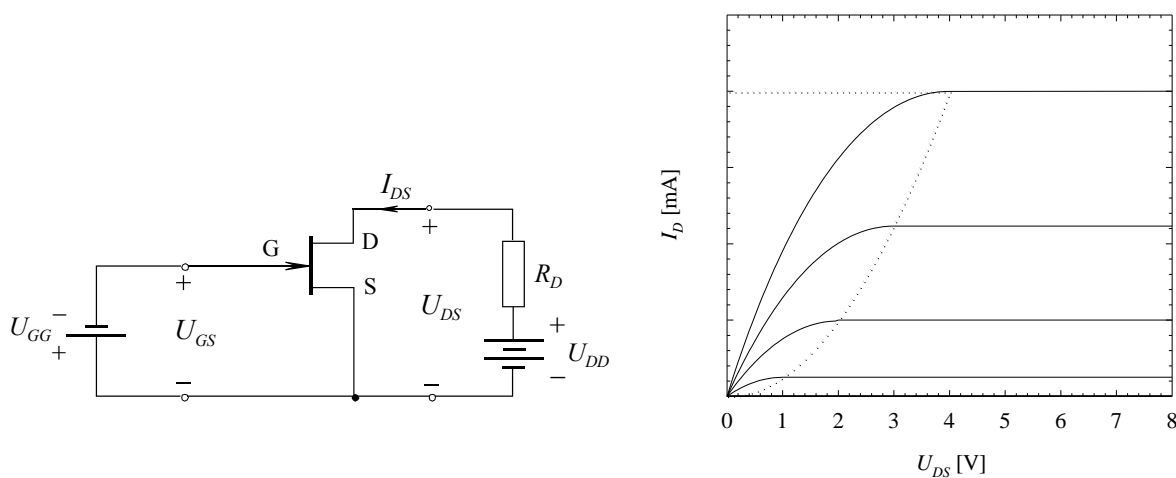4. Channel of junction FET-a is doped with $N_D = 4 \times 10^{15}$ cm^{-3} , channel thickness is $D = 2,425$ μ m, diffusion voltage U_D at pn -junctions is 0,7 V, largest saturation current is $I_{DSS} = 4$ mA. Calculate and draw in graph missing current I_D , voltages U_{GS} and U_{DSSat} . Draw also resistive load line determine the quiescent point. Other data: $U_{DD} = 8$ V, $U_{GG} = 1$ V and $R_D = 2$ k Ω .



Time limit: 60 minutes. One page with basic equations allowed.