


Written exam at the subject  
**SEMICONDUCTOR DEVICES**  
 (ELEMENTI POLPREVODNIŠKE ELEKTRONIKE)  
 1<sup>st</sup> Bologna grade – 2<sup>nd</sup> year – Electronics – AE  
 26. 1. 2016

1. Determine semiconductor type for a sample/piece of crystalline Si, which contains homogeneously distributed acceptor impurities of the following concentration  $N_A = 5 \times 10^{17} \text{ cm}^{-3}$ . Calculate the energy difference (in eV) between the actual and intrinsic Fermi level and sketch energy band diagram. Calculate the specific conductivity of the sample.

(Data:  $T = 300 \text{ K}$ ,  $\mu_n = 1300 \text{ cm}^2(\text{Vs})^{-1}$ ,  $\mu_p = 450 \text{ cm}^2(\text{Vs})^{-1}$ ).

**(Solution: p-type,  $U_T = 25,88 \text{ mV}$ ;  $E_F - E_{Fi} = -0,459 \text{ eV}$ ;  $\sigma = 36 \text{ S/cm}$ )**

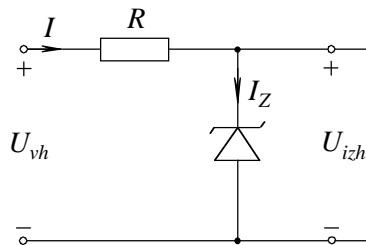
2. In a simple voltage stabilizer in the picture below specify the value of the resistor  $R$  so that at the input voltage  $U_{vh} = 24 \text{ V}$  the current through the diode equals  $I_Z = 10 \text{ mA}$ . The diode has parameters  $U_{Z0} = 12 \text{ V}$  and  $r_Z = 15 \Omega$ . Take both parameters into account and determine the value of the output voltage  $U_{izh}$  for the given input voltage.



**(Solution:  $R = 1185 \Omega$ ,  $U_{izh} = 12,15 \text{ V}$ )**

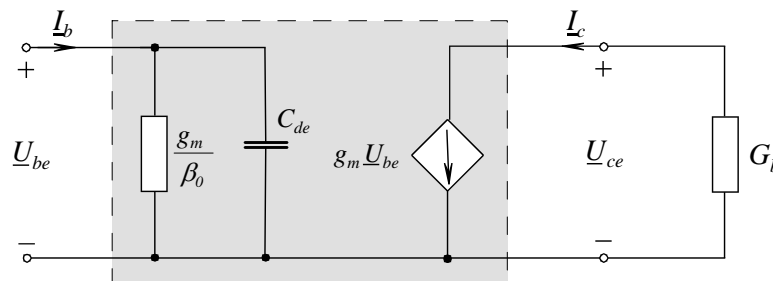3. Using the given model of a bipolar transistor at high frequencies, calculate the (absolute) value of the current gain of the transistor at the frequency  $f = 10 \text{ MHz}$ .


(Data:  $g_m = 40 \text{ mS}$ ,  $\beta_0 = 75$ ,  $C_{de} = 6 \text{ pF}$ ).



**(Solution:  $|\beta_f| = 61,2$ )**

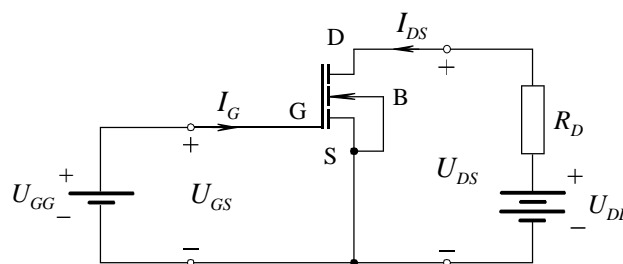4. In the given circuit with a MOS transistor determine the resistance  $R_D$  so that the output voltage  $U_{DS}$  equals to half of the supply voltage  $U_{DD}$ . Draw the equivalent circuit for small signals, determine the parameter  $g_{21}$  and calculate the voltage gain of the circuit, which is defined as the ratio of small amplitude AC component of output to input voltage  $A_u = u_{ds}/u_{gs}$ .

(Podatki:  $U_{DD} = 12 \text{ V}$ ,  $U_{GG} = 5 \text{ V}$ ,  $U_T = 3 \text{ V}$ ,  $C_0 \mu_n = 2 \text{ mAV}^{-2}$ ,  $W/L = 8$ )



**(Solution: saturation,  $I_D = 32 \text{ mA}$ ,  $R_D = 188 \Omega$ ,  $g_{21} = 32 \text{ mS}$ ,  $A_u = -6$ )**

You have 60 minutes, you are allowed to use the sheet with basic formulas and constants. The results are expected to be communicated on tomorrow morning via e-mail.